

Name	Muhammad Asad
Reg. #	2019-EE-383
Marks	

Experiment # 13

Open Ended Lab

Design a Sequential Circuit to Check Parity for Error Detection in a Communication System


Objective:

- *Designing of a digital system based on background knowledge*

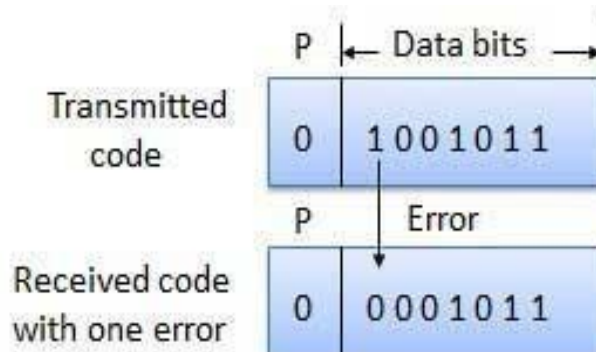Problem Statement:

In information theory and coding theory with applications in computer science and telecommunication, **error detection** and **correction or error control** are techniques that enable reliable delivery of digital data over unreliable communication channels. Many communication channels are subject to channel noise, and thus errors may be introduced during transmission from the source to a receiver. Error detection techniques allow detecting such errors to avoid false reception of information.

One of the error detection techniques is parity checker. This scheme is used to detect 1-bit error.




As a design engineer, you are required to design a sequential circuit that can check the **odd parity** of input bit stream received at receiver. Total number of 1's should be odd for error-free reception, in this case circuit should generate output **0**. If total number of 1's is even, it will generate output **1**. Your circuit will have one input and one output as shown in the state table below:

Input	Present state (PS)	Next state (NS)/Output
0	0	0
0	1	1
1	0	1
1	1	0

Input stream (start from right) **1 0 0 1 1 0 1 0 1 1 1 0** should be provided to the system using serial register.

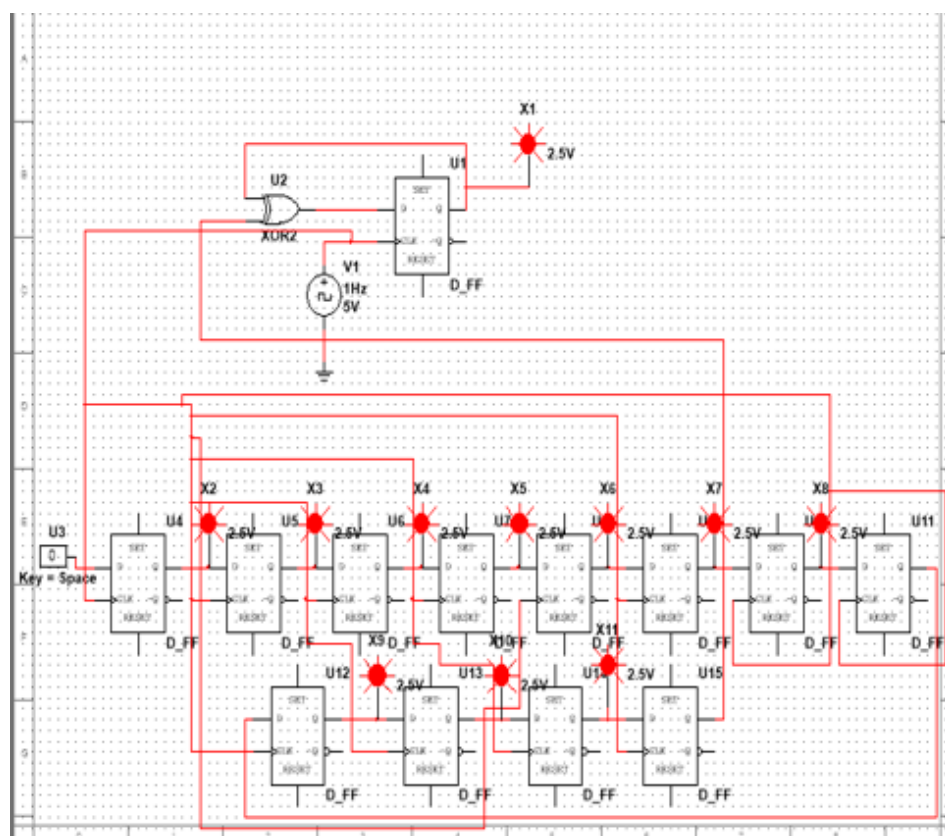1. Using D-flipflop, design the circuit diagram (*perform all the calculations and upload scanned copy at the end of the 1st hour*)
2. Write the HDL code for the circuit (*upload Verilog code file at the end of lab*)
3. Implement the circuit and check the results (*upload the circuit and results at the end of the lab*)
4. **Submit a complete report before dead line**



```

module lab13 (A,CLK,B)
input A,CLH;
output B;
xg B;
initial
begin
B=0;
end
always @(posedge CLK)
case (A)
1'b0 : B<= 0;
1'b1 : B<= 1;
endcase
endmodule
module gate(C,D,E):
input C,D;
output E;
xor x1(E,C,D);
endmodule
module test_Laasb13():
reg A,CLK,C;
win [0:13]B;
laL13b1 (A,CLF,B[0];
Lab13b2 (B[0],CIA,B[1]);
LaL13 b3 (B[1],CIA,B[2])a
LaL13 b4 {B[2]CIX,B[3]} â=1: 010:
LaL13 b5 (B[3]CIE,B[4])a é=0: 010:
LaL13 b6 (B[4]CIE,B[5]: A=1: #10:
LaL13 b7 (B[5]CIX,B[6]: A=0: #10:
LaL13 b9 (B[6]CIX,B[7]: é=1: #10:
LaL13 bS (B[7]CIX,B[9]: A=1: #10:
LaL13 b10 (B[9]CIE,B[S]: â=0: #10:
lab13b11 (B[S],CIF,B[10]); é=0: #10:
lab13b12 (B[10],CLF,B[11]); A=1: #10;
initial begin
C=0;
end
endmodule
end
lab13 b2 (B[0],CLK,B[1]);
LaL13 b3 (B[1]CIE,B[2]:
lab13 b4 (B[2],CIF,B[3]);
Lab13b5 (B[3],CLF,B[4]:
Lat13b6 (B[4],CLK,B[5]:
Lat13 b7 (B[5]CIE,B[6]:
LaL13 b9 (B[6]CIE,B[7]:
LaL13 bS (B[7]CIF,B[9]:
LaL13b10 (B[9]CIX,B[S] *1
Lab13 b11 (B[S],CLK,B[10]):
LaL13 b12 (B[10],CIA,B[11]Q
initial begin
C=0;
end
gate g1 (B[11],C,B[12]):
Lab13 b13 (B[12],CLH,B[13]):
initial
begin
CLK= 0;
end
always é5CLK=-CLK;
initial
begin
â=0; #10;
â=1: 10:
â=1: 10:
â=1: 010:
é=0: 010:
A=1: #10:
A=0: #10:
é=1: #10:
A=1: #10:
â=0: #10:
é=0: #10:
A=1: #10;
end
endmodule

```

